

STMicroelectronics
Systolic Array for Applying Matrix Multiplication

Muhammed Adel Ahmed El-Sayed

Table of Contents

Introduction.....	4
Design Implementation.....	4
Processing Element (PE) Design	4
PE Inputs and Outputs.....	5
PE Internal Operation.....	5
Systolic Array Module Design.....	7
Systolic Data Flow Principles	7
Systolic Array Interface and internal buses	8
Systolic PE Array Generation	9
Input Distribution Logic.....	10
Systolic Matrix Multiplication Example (N= 3)	12
Architecture Diagram	12
Design Verification	14
Verification Objectives	14
Verification Methodology	14
Test Cases	14
1. 2x2 Matrices	14
2. 3x3 Matrices.....	15
3. 4x4 Matrices	17
4. 5x5 Matrices	18
Conclusion	20

Table of Snippets


Snippet 1: PE I/O interface.....	5
Snippet 2: PE internal operation.....	6
Snippet 3: SA Interface	8
Snippet 4: The slices wires that hold the inputs.....	9
Snippet 5: Connections between buses and the wires which hold input matrixes.....	9
Snippet 6: Generation of PEs inside the SA.....	9
Snippet 7: The initialization of signals during negedge of rst_n	10
Snippet 8: Shifting Pattern	11
Snippet 9: The initialization when new input data	11
Snippet 10: The snippet that indicate what happen when we finish the inputs.....	11
Snippet 11: The assignment of matric_c_out	12
Snippet 12: Initialization Test	14
Snippet 13: Log of 2x2	15
Snippet 14: 3x3 Log	16
Snippet 15: 4x4 Log file.....	18
Snippet 16: 5x5 Log file.....	19

Table of Figures

Figure 1 :Top-level PE	4
Figure 2: Hardware structure of PE	6
Figure 3:Block Diagram of a PE	6
Figure 4: SA Top-Level	7
Figure 5: SA Data Flow	7
Figure 6: An explanation of the connections happens during the generation of PEs	10
Figure 7: An explanation of how inputs enter the PE	10
Figure 8 :Block diagram of simple 2x2 Systolic Array	13
Figure 9: An abstraction of everything about the design.....	13
Figure 10: 2x2 Test case indicating the enable of valid_in and data entry flow	
Figure 11: 2x2 Test case indicating rising of valid_out	
Figure 12: 3x3 Test case indicating the enable of valid_in and data entry flow	
Figure 13: 3x3 Test case indicating rising of valid_out	
Figure 14: 3x3 test case indicating the output transition	

Introduction

In this document, I will show the architecture and operation of a systolic array designed for matrix multiplication. Systolic arrays are specialized parallel computing architectures that excel at computationally intensive tasks like matrix operations by employing a network of interconnected processing elements (PEs) that process data in a pipelined fashion. This design leverages the inherent parallelism of matrix multiplication to achieve high throughput and efficiency. As shown in gif 1, an abstract overview about the operation of systolic array.

 

Design Implementation

Processing Element (PE) Design

Processing Element (PE), a fundamental building block responsible for performing the multiply-accumulate operation. Each PE is designed to handle a single element multiplication and accumulate the result, while also passing data to its neighboring PEs. As shown in Fig the top-level PE design indicating the interface I/O ports.

 


Figure 1 :Top-level PE

PE Inputs and Outputs

The following table indicate the interface ports with an abstract description of its operation.

Signal	Direction	Width	Description
clk	Input	1 bit	Global clock signal that synchronizes all operations within the PE.
rst_n	Input	1 bit	Active-low asynchronous reset. When asserted, initializes the PE's internal registers to zero.
a_left	Input	DATAWIDTH bits	Signed input from the PE on the left; carries an element of matrix A.
b_top	Input	DATAWIDTH bits	Signed input from the PE above; carries an element of matrix B.
a_right	Output	DATAWIDTH bits	Signed output to the PE on the right; forwards a_left after a one-clock delay.
b_bottom	Output	DATAWIDTH bits	Signed output to the PE below; forwards b_top after a one-clock delay.
final_result	Output	2 × DATAWIDTH bits	Signed accumulated partial-sum (product) for this PE, contributing to the final C matrix element.

Table 1: PE I/O Ports

As shown in snippet code 1, the interface ports parametrized with DATAWIDTH 16-bit.

```
// Systolic Processing Element (PE)
// This module performs multiply-accumulate operations and forwards data to
// neighbors.
module systolic_pe #(
    parameter integer DATAWIDTH = 16 // Width of input operands
)(
    input wire          clk,           // Clock signal
    input wire          rst_n,         // Active-low reset
    input wire signed [DATAWIDTH-1:0] a_left, // Input data from left neighbor
    input wire signed [DATAWIDTH-1:0] b_top,  // Input data from top neighbor
    output reg signed [DATAWIDTH-1:0] a_right, // Output data to right neighbor
    output reg signed [DATAWIDTH-1:0] b_bottom, // Output data to bottom neighbor
    output wire signed [2*DATAWIDTH-1:0] final_result // Output accumulated result
);
```

Snippet 1: PE I/O interface

PE Internal Operation

As shown in snippet code , the primary internal component of the PE is the accumulator register, which is double wide to prevent overflow during the multiplication and accumulation.

The operation of the PE is governed by a synchronous `always_ff`.

When assert (`rst_n`), all outputs (`a_right` , `b_bottom`) and the cleared to zero thus the PE zero.

In normal operation (when accumulator is `rst_n` is high), the PE performs two main functions:

1. Data Forwarding: The `a_left` input is registered and the `b_top` input is registered then passed to `a_right` , and `b_bottom` . This ensures that data propagates, maintaining synchronization across all PEs.
2. Multiply-Accumulate (MAC) Operation: This involve multiplying the current `a_left` and `b_top` inputs and adding the product to the accumulator . As shown in the snippet code. This operation is fundamental to matrix multiplication.

```

// Internal accumulator for partial sums (size double DATAWIDTH)
reg signed [2*DATAWIDTH-1:0] accumulator;
// Connect internal accumulator to final output
assign final_result = accumulator;
// Sequential logic: on clock edge or reset
always_ff @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        // On reset, clear outputs and accumulator
        a_right <= 0;
        b_bottom <= 0;
        accumulator <= 0;
    end else begin
        // Forward input data to neighboring PEs
        a_right <= a_left;
        b_bottom <= b_top;
        // Perform multiply-accumulate: update dot-product term
        accumulator <= accumulator + (a_left * b_top);
    end
end

```

Snippet 2: PE internal operation

The final_result output is assigned the value of the accumulator. The design implies that the accumulation continues over multiple clock cycles as new a_left and b_top values arrive.

The schematic shown in fig to show the architecture detailed component.

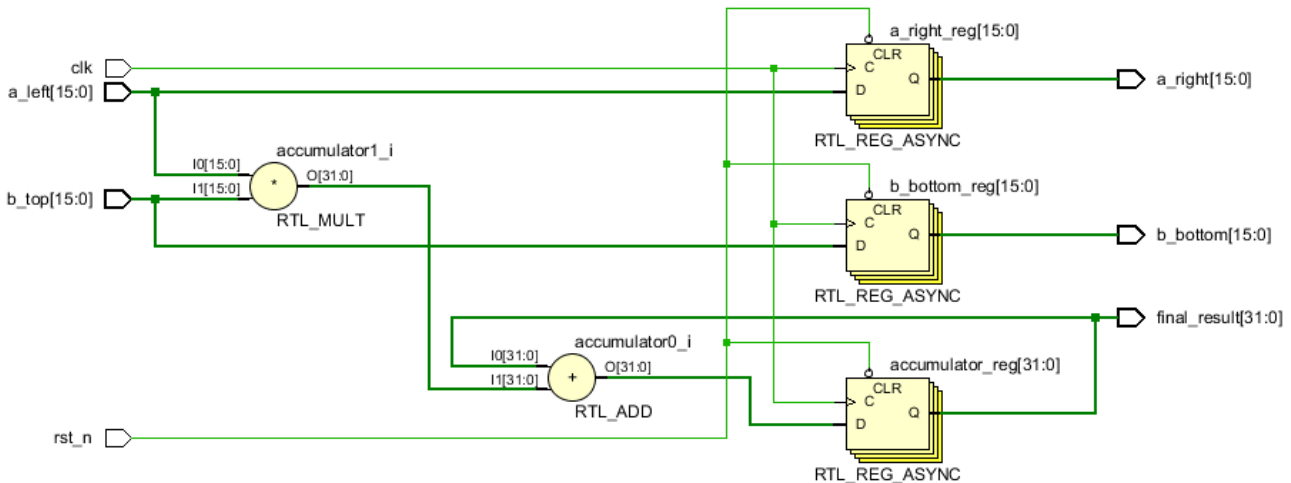


Figure 2: Hardware structure of PE

As shown in fig, the Architecture diagram shows the architecture of the implementation of PEs.

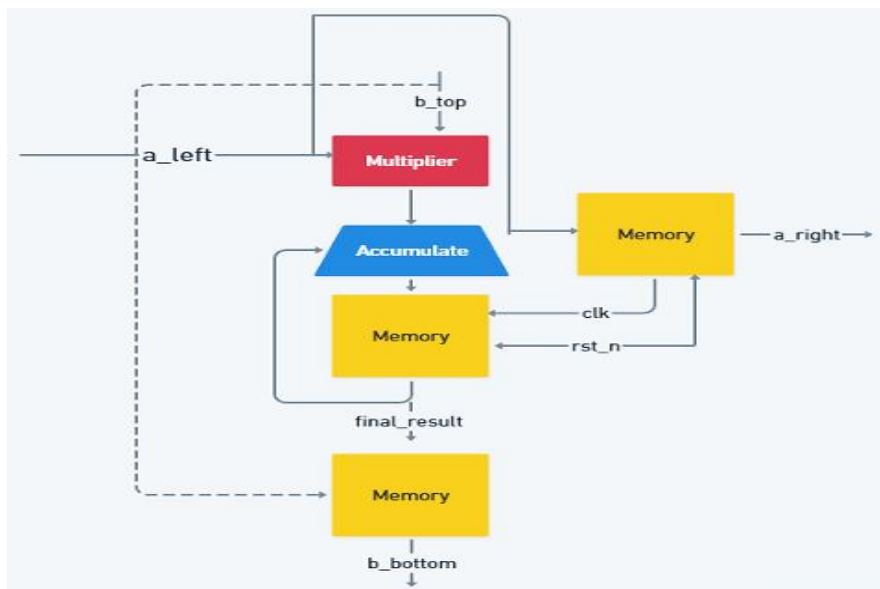


Figure 3:Block Diagram of a PE

Systolic Array Module Design

The systolic_array orchestrates the interaction of multiple systolic_pe instances to perform matrix multiplication. It handles the input distribution of matrices A and B, manages the data flow through the array, and collects the final results to form matrix C. The given fig shows the top-level of the design indicating the I/O ports interface.

Diagram


 


Figure 4: SA Top-Level

Systolic Data Flow Principles

1. **Talk Only to Your Neighbors:** Each unit sends and receives data just from the ones right beside it.
2. **Clock-Driven Data:** Every tick, data moves one step through the grid like a pulse.
3. **Continuous Pipelining:** New data enters each cycle while old data keeps flowing out—no idle time.
4. **Combine as You Go:** Partial results pass along and get added up without big memories.

Figure 5: SA Data Flow

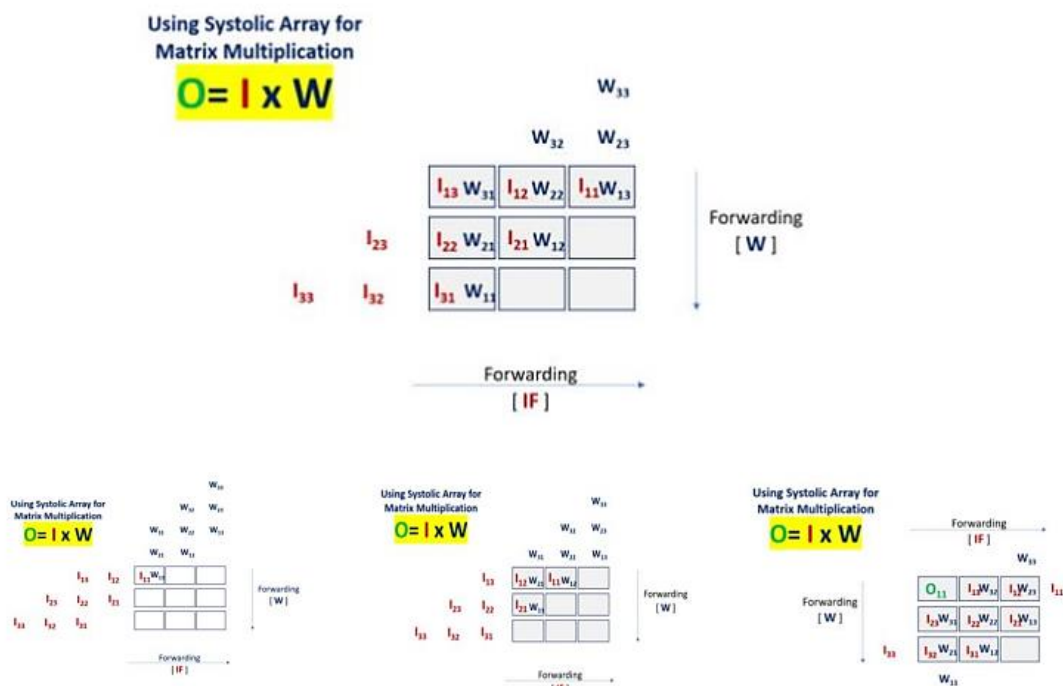

Systolic Array Interface and internal buses

The following table indicate the interface ports with an abstract description of its operation.

Signal	Direction	Width	Description
clk	Input	1 bit	Global clock signal.
rst_n	Input	1 bit	Global active-low asynchronous reset signal.
valid_in	Input	1 bit	Control signal indicating that new input data for matrix_b_in is available this cycle.
matrix_a_in	Input	$N_SIZE \times DATAWIDTH$ bits	Carries a row or column of matrix A (distribution depends on your tiling strategy).
matrix_b_in	Input	$N_SIZE \times DATAWIDTH$ bits	Carries a row or column of matrix B.
valid_out	Output	1 bit	Pulses high for one cycle when the entire array has finished computing and matrix_c_out holds a valid result.
matrix_c_out	Output	$N_SIZE \times 2 \times DATAWIDTH$ bits	Carries the resulting matrix C; the $2 \times DATAWIDTH$ factor accounts for bit-width growth due to accumulation in the PEs.

Table 2: SA I/O Ports

As shown in snippet code , the interface ports parametrized with DATAWIDTH 16-bit and N_SIZE for matrixes dimension.

```
module systolic_array #(
    parameter integer DATAWIDTH = 16, // Bit-width for each PE
    parameter integer N_SIZE      = 5  // Matrix dimension (N x N)
)(
    input wire                clk,           // Clock signal
    input wire                rst_n,         // Active-low reset
    // Input: new row/column injected when valid_in is high
    input wire                valid_in,
    input wire signed [N_SIZE*DATAWIDTH-1:0] matrix_a_in,
    input wire signed [N_SIZE*DATAWIDTH-1:0] matrix_b_in,
    output logic              valid_out,
    output logic signed [N_SIZE*2*DATAWIDTH-1:0] matrix_c_out
);
```

Snippet 3: SA Interface

The design utilizes several internal wires and registers to manage data flow:

- $a_bus[0:N_SIZE][0:N_SIZE - 1] \rightarrow$ 2D array of wires carrying matrix A elements horizontally between PEs, As shown in fig.
- $b_bus[0:N_SIZE - 1][0:N_SIZE] \rightarrow$ 2D array of wires carrying matrix B elements vertically between PEs, As shown in fig.

Snippet 5: Connections between buses and the wires which hold input matrixes

```
genvar i, j;
generate
  for (i = 0; i < N_SIZE; i = i + 1) begin : INPUT_CONNECTIONS
    // Left boundary feeds A values into first column
    assign a_bus[i][0] = valid_in ? a_slice[i] : '0;
    // Top boundary feeds B values into first row
    assign b_bus[0][i] = valid_in ? b_slice[i] : '0;
  end
endgenerate
```

- $result_bus[0:N_SIZE - 1][0:N_SIZE - 1] \rightarrow$ 2D array of wires carrying the final_result from each PE. These results are eventually combined to form matrix_c_out .
- a_input_regs and $b_input_regs \rightarrow$ Registers used to temporarily hold and distribute input data to the first row and column of PEs.
- $delay \rightarrow$ A counter used to manage the timing and synchronization of input data distribution, ensuring that data arrives at the correct PE at the correct time for the systolic operation.
- a_slice and $b_slice \rightarrow$ Helper wires used for bit-slicing the wide and matrix_b_in buses into individual matrix_a_in DATAWIDTH-bit elements for distribution to the PEs.

```
// Generate bit slicing for input matrices
genvar k;
generate
  for (k = 0; k < N_SIZE; k = k + 1) begin : SLICE_GEN
    // Extract each DATAWIDTH-bit element from flattened inputs
    assign a_slice[k] = matrix_a_in[(k+1)*DATAWIDTH-1:k*DATAWIDTH];
    assign b_slice[k] = matrix_b_in[(k+1)*DATAWIDTH-1:k*DATAWIDTH];
  end
endgenerate
```

Snippet 4: The slices wires that hold the inputs

Systolic PE Array Generation

As shown in snippet code , the core of the systolic_array module is a nested N_SIZE by N_SIZE that instantiates PEs modules. Each PE (pe_inst) is connected to its neighbors using the a_bus and b_bus wires, forming a grid. The at (i, j) is connected to a_right of b_bottom of a_left input of a PE (i, j-1), and b_top is connected to (i-1, j) .

```
generate
  for (i = 0; i < N_SIZE; i = i+1) begin : ROWS
    for (j = 0; j < N_SIZE; j = j+1) begin : COLS
      systolic_pe #(
        .DATAWIDTH(DATAWIDTH)
      ) pe_inst (
        .clk          (clk),
        .rst_n        (rst_n),
        .a_left       (a_bus[i][j]),      // Input from left
        .b_top        (b_bus[i][j]),      // Input from top
        .a_right      (a_bus[i][j+1]),    // Output to right
        .b_bottom     (b_bus[i+1][j]),    // Output to bottom
        .final_result(result_bus[i][j]) // Partial dot-product
      );
    end
  end
endgenerate
```

Snippet 6: Generation of PEs inside the SA

As shown in fig, this clarifies the connection between PEs through **a_bus** and **b_bus** thus this creates the characteristic systolic data flow.

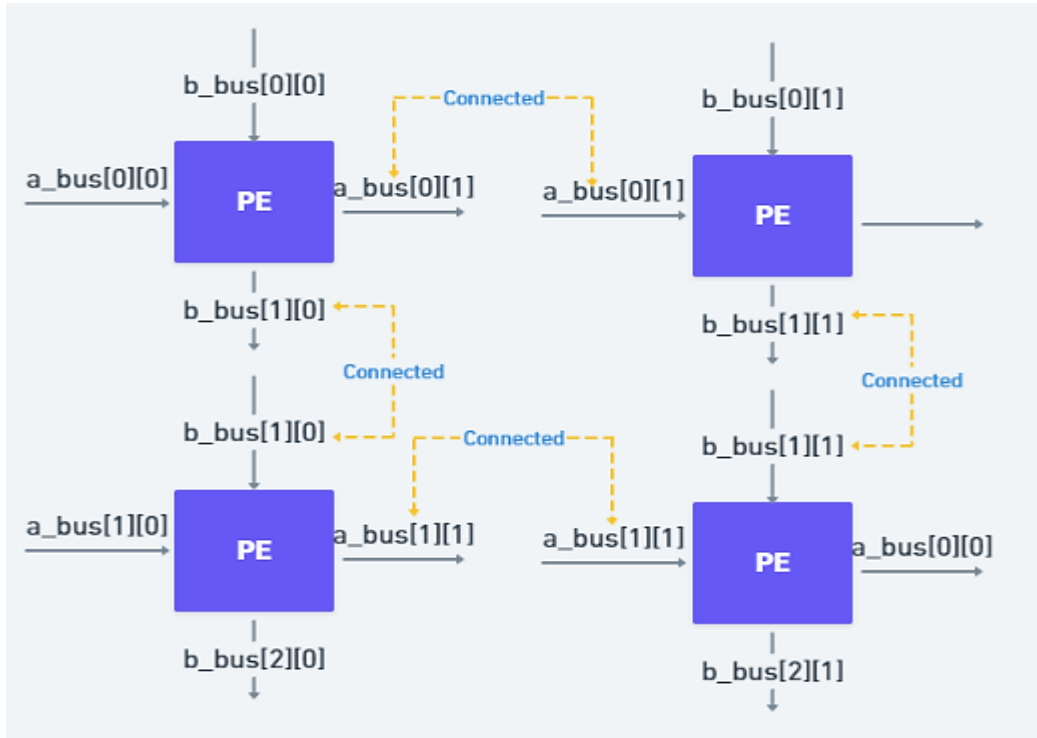


Figure 6: An explanation of the connections happens during the generation of PEs

Input Distribution Logic

This logic is responsible for feeding the **matrix_a_in** and **matrix_b_in** data into the array in a staggered fashion, which is critical for the correct operation of a systolic array for matrix multiplication.

During the initial cycles (**rst_n** is asserted), I initialize the registers that used to temporarily hold and distribute input data to the first row and column of PEs, initialize the timing counter **delay** which make the first element of **matrix_a_in** enter the PEs and delay the other elements and so on as shown in fig and initialize the counter **c** which will enable the **valid_out** after **N_SIZE + 1** thus a valid output you can take is available.

```
// Main control for distributing inputs and generating valid_out
always @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin // Initialize registers and counters on reset
        for (integer i = 0; i < N_SIZE; i = i + 1) begin
            a_input_regs[i] <= 0;
            b_input_regs[i] <= 0;
        end
        valid_d <= 0;
        delay <= 1;
        c <= N_SIZE+1;
    end
end
```

Snippet 7: The initialization of signals during negedge of **rst_n**

 


Figure 7: An explanation of how inputs enter the PE

When `valid_in` is asserted, the module processes the incoming `matrix_a_in` and `matrix_b_in` by slicing them into individual elements and directing them to the appropriate `a_input_regs` and `b_input_regs` based on the current delay count so this ensures that the data is correctly aligned for the PEs. (controlled by `delay <= N_SIZE`), elements are loaded into the PEs along the anti-diagonal at which the elements in the column loaded one by one each cycle meaning that at first cycle in 3x3 matrixes let say 1 0 0 and `delay = 1`, in the next cycle 1 1 0 `delay = 2`, third cycle 1 1 1 `delay = 3` so the next cycle we expected to fill the zeros before the elements so let say 0 1 1 after that 0 0 1 then 0 0 0, as shown in code snippet.

Shifting Pattern: In subsequent cycles (controlled by `delay <= 2 * N_SIZE - 1`), the input data shifts, allowing new elements to enter the array and propagate through the PEs. The `shift_offset` variable helps in correctly indexing the `a_slice` and `b_slice` to feed the PEs, as shown in fig that illustrate that when we enter 4x4 matrix so we expect that we will shift by 7 cycles.

```
// Phase 1: load diagonal elements in cycles 1 to N_SIZE
if (delay <= N_SIZE) begin
    for (integer i = 0; i < delay; i = i + 1) begin
        a_input_regs[i] <= a_slice[i];
        b_input_regs[i] <= b_slice[i];
    end
    valid_d <= 0; // No valid output yet
    c <= N_SIZE+1;
end
// Phase 2: shift inputs in cycles N_SIZE+1 to 2*N_SIZE-1
else if (delay <= 2*N_SIZE-1) begin
    shift_offset = delay - N_SIZE;
    for (integer i = shift_offset; i < N_SIZE; i = i + 1) begin
        a_input_regs[i] <= a_slice[i-shift_offset];
        b_input_regs[i] <= b_slice[i-shift_offset];
    end
end
end
```

Snippet 8: Shifting Pattern

As shown in snippet code, when a new data arrives so clear all input temporally regs as to hold the new data from the input's matrixes.

```
else if (valid_in) begin
    // When new data arrives, clear input regs first
    for (integer i = 0; i < N_SIZE; i = i + 1) begin
        a_input_regs[i] <= '0;
        b_input_regs[i] <= '0;
    end
end
```

Snippet 9: The initialization when new input data

When the counter `delay` reach `N_SIZE + 1` so we expect that we finish inputting the two matrix and its time to disenable the `valid_in` to enable the `valid_out` so we can get the output row by row by each cycle in the same time decreasing `c` counter as after reach the final row we disenable the output as the design finish its computation at this time we initialize the counter again.

```
else if (delay == N_SIZE+1) begin
    // After loading, generate valid pulses and track rows
    if (c > 1) begin
        c <= c-1;
        valid_d <= 1; // Pulse valid while draining results
    end
    else begin
        // Reset for next operation
        delay <= 1;
        valid_d <= 0;
        c <= N_SIZE+1;
    end
end
```

Snippet 10: The snippet that indicate what happen when we finish the inputs

The `result_bus` collects the results, `final_result` results from each PE. An `always_comb` block is used to combine these individual PE results into the output `matrix_c_out` bus when `valid_out` is asserted. The `valid_out` signal enabled after the entire array has completed its computation, indicating that, valid result of the matrix multiplication.

```
// Assemble final output matrix when valid_out is high
always_comb begin
    if (valid_out) begin
        for (integer s = 0; s < N_SIZE; s = s + 1) begin
            matrix_c_out[s*2*DATAWIDTH +: 2*DATAWIDTH] = result_bus[N_SIZE-c][s];
        end
    end
    else begin
        matrix_c_out = '0; // Default output when not valid
    end
end
```

Snippet 11: The assignment of `matrix_c_out`

Systolic Matrix Multiplication Example (N= 3)

I'll illustrate with a 3x3 matrix multiplication. The input data streams for A and B are fed into the array in a staggered manner to ensure that the correct elements arrive at the correct PEs.

Consider the elements a_{ij} from matrix A and b_{ij} from matrix B. The PE at position (i, j) will compute the sum of products that contributes to C_{ij} .

- Initial Phase: The first elements (e.g., a_{00} and b_{00}) enter the top-left PE (0,0). They are multiplied, and the product is added to the accumulator of PE(0,0).
- Propagation: In the next clock cycle, a move to PE(0,1) and b moves to PE(1,0). Simultaneously, new elements (e.g., a_{01} and b_{10}) enter PE(0,0) and PE(1,0) respectively, and a_{10} and b_{01} enter PE(0,1) and PE(1,0).
- Staggered Input: The `valid_in` signal and the internal that the inputs `matrix_a_in` and `delay counter` ensure `matrix_b_in` are sliced and fed into the array such that elements that need to interact arrive at the same PE at the same time.
- The `final_result` from each PE, the results for matrix C will emerge from the PEs in a staggered fashion. The `valid_out` signal indicates when the complete `matrix_c_out` is available.

Architecture Diagram

As shown in fig, an abstraction block diagram that show:

- Components in the design.
- Output signals.
- Input signals.
- Abstracted Data Flow.
- PE structure component.

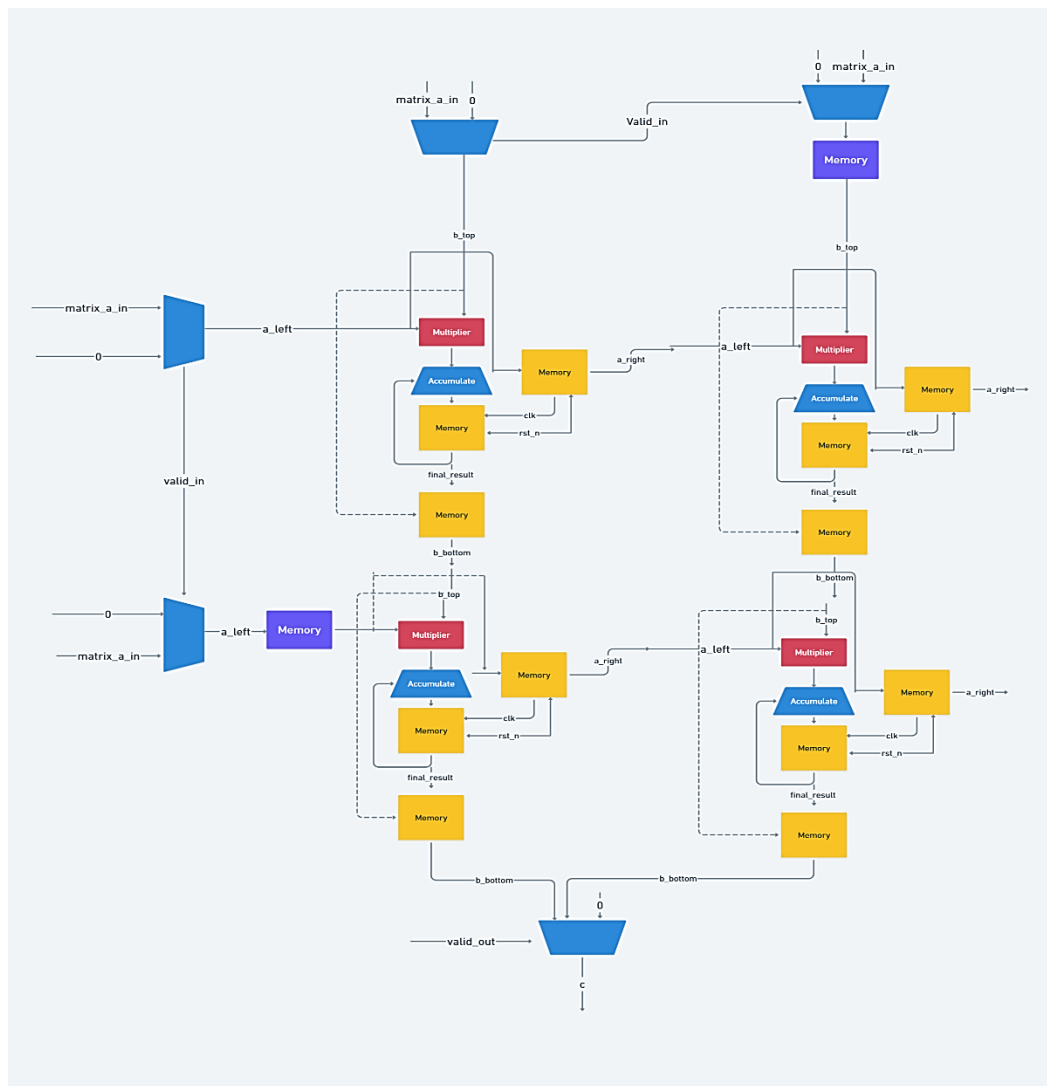


Figure 8 :Block diagram of simple 2x2 Systolic Array

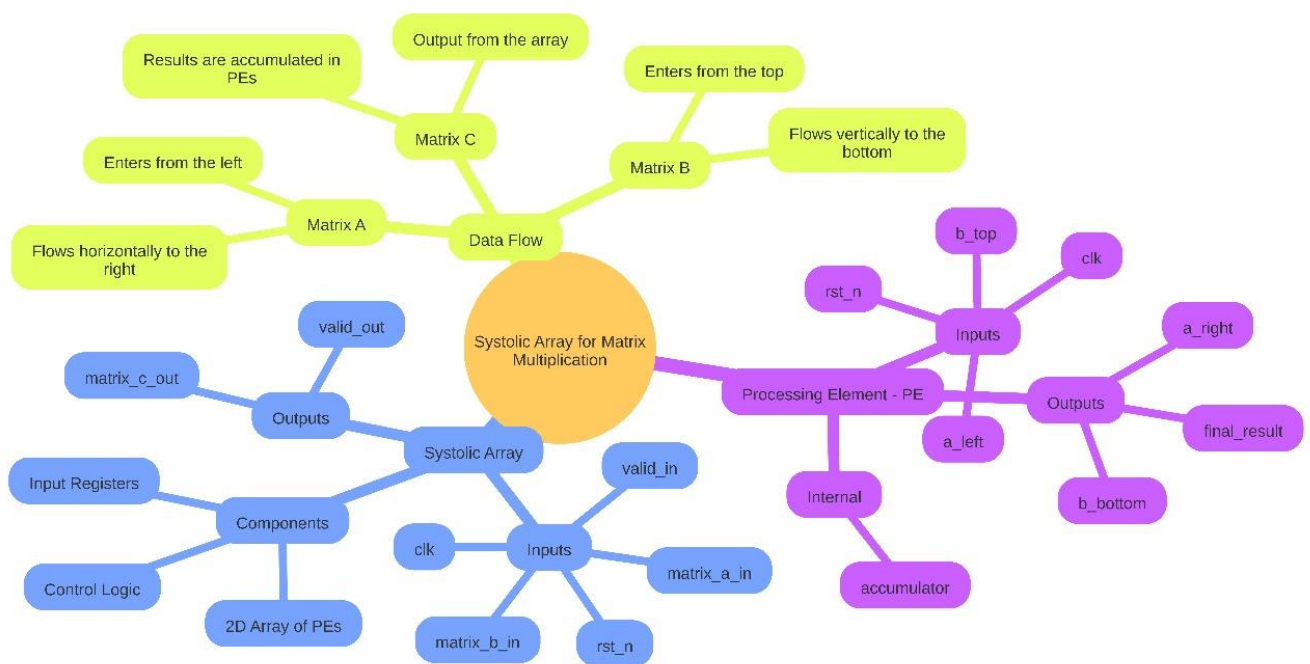


Figure 9: An abstraction of everything about the design

Design Verification

Verification Objectives

- Verify that the systolic array performs accurate matrix multiplication for all supported matrix sizes (2x2, 3x3, 4x4, 5x5, .etc.) based on N_SIZE, Confirming that the design scales correctly for different N_SIZE parameters.
- Ensure proper data flow synchronization across all processing elements (PEs) in the array.
- Validate correct handshaking between input/output interfaces and internal processing units.

Verification Methodology

Directed Testing : Specific test cases targeting known corner cases and boundary conditions

```
// Generic task to initialize test matrices
task automatic init_test_matrices;
  integer i, j;
  begin
    // Matrix A: Sequential values starting from 1
    for (i = 0; i < N_SIZE; i = i + 1) begin
      for (j = 0; j < N_SIZE; j = j + 1) begin
        matrix_a[i][j] = i * N_SIZE + j + 1;
      end
    end

    // Matrix B: Reverse sequential values
    for (i = 0; i < N_SIZE; i = i + 1) begin
      for (j = 0; j < N_SIZE; j = j + 1) begin
        matrix_b[i][j] = N_SIZE * N_SIZE - (i * N_SIZE + j);
      end
    end
  end
endtask
```

Snippet 12: Initialization Test

Test Cases

1. 2x2 Matrices

As shown in fig , when the user has to apply the inputs matrixes then the valid_in will be enabled so at each posedge of cycles the inputs will entering.

When the inputs are finished so the valid_in will dis enabled


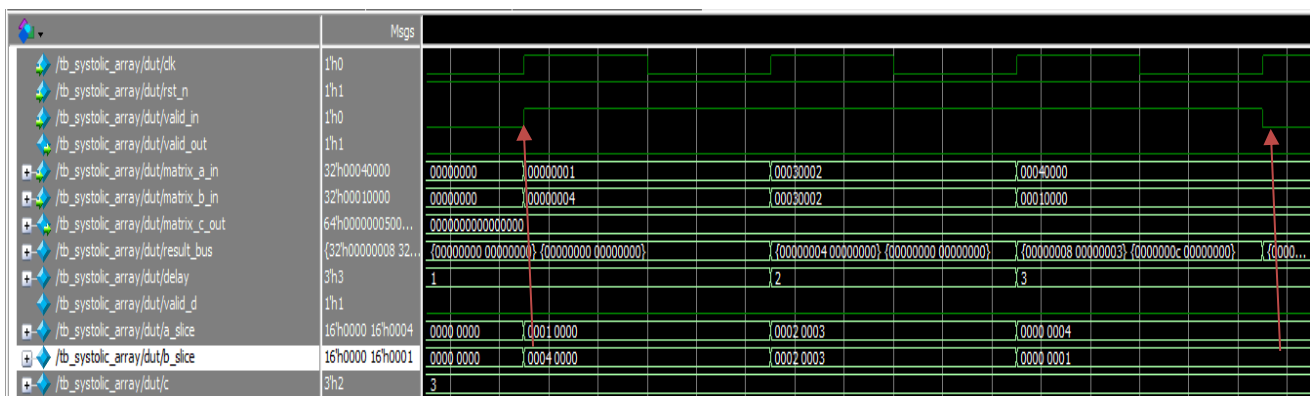


Figure 10: 2x2 Test case indicating the enable of valid_in and data entry flow

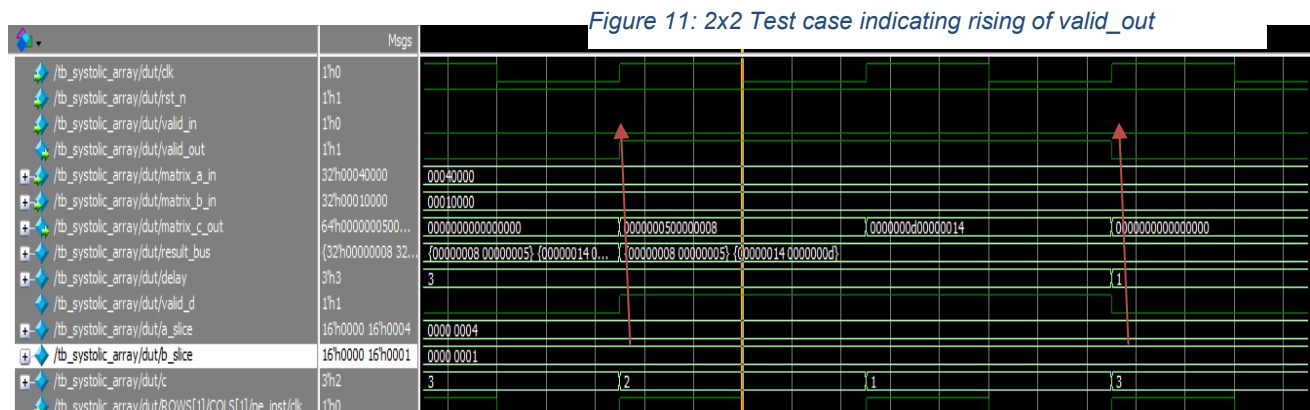As shown in fig , when the inputs are finished the valid_out will be enabled so that the design will output matrix c row by row at each posedge then when the output finished its valid output multiplied then the valid_out will dis enabled again.



The Output Results as shown in the log file indicating the inputs matrixes and the expected and actual results so correct output results.

```
# --- Test Case: 2x2 Matrix Multiplication ---
# Matrix A:
#   1  2
#   3  4
# Matrix B:
#   4  3
#   2  1
# Expected Result (A * B):
#   8   5
#  20  13
#
# Collecting matrix outputs...
# Row 0 collected: 0000000500000008
# Row 1 collected: 0000000d00000014
# All 2 rows collected successfully!
# === Output Results ===
# Collected Matrix Rows (Raw Hex):
# Row 0: 0000000500000008
# Row 1: 0000000d00000014
# Actual Result Matrix:
#   8   5
#  20  13
# SUCCESS: All results match expected values!
```

Snippet 13: Log of 2x2

2. 3x3 Matrices

As shown in fig , when the user has to apply the inputs matrixes then the valid_in will be enabled so at each posedge of cycles the inputs will entering.

When the inputs are finished so the valid_in will dis enabled

 


Figure 12: 3x3 Test case indicating the enable of valid_in and data entry flow

As shown in fig, the inputs keep entering while valid_in enabled and valid_out disenabled.



Figure 13: 3x3 Test case indicating rising of valid_out

As shown in fig , when the inputs are finished the valid_out will be enabled so that the design will output matrix c row by row at each posedge then when the output finished its valid output multiplied then the valid_out will dis enabled again.

 


Figure 14: 3x3 test case indicating the output transition

The rows are got in hex in the fig:

- 00000012000000180000001e → 30 24 18
- 000000360000004500000054 → 84 69 54
- 0000005a000000720000008a → 138 114 90

Which are the expected results.

The Output Results as shown in the log file indicating the inputs matrixes and the expected and actual results so correct output results.

```
# --- Test Case: 3x3 Matrix Multiplication ---
# Matrix A:
# 1 2 3
# 4 5 6
# 7 8 9
# Matrix B:
# 9 8 7
# 6 5 4
# 3 2 1
# Expected Result (A * B):
# 30 24 18
# 84 69 54
# 138 114 90
# === Output Results ===
# Actual Result Matrix:
# 30 24 18
# 84 69 54
# 138 114 90
# --- Verification ---
# SUCCESS: All results match expected values!
```


3. 4x4 Matrices

As shown in fig , when the user has to apply the inputs matrixes then the valid_in will be enabled so at each posedge of cycles the inputs will entering.

When the inputs are finished so the valid_in will dis enabled

 


Figure 15:4x4 Test case indicating the enable of valid_in and data entry flow

As shown in fig, the inputs keep entering while valid_in enabled and valid_out disenabled.

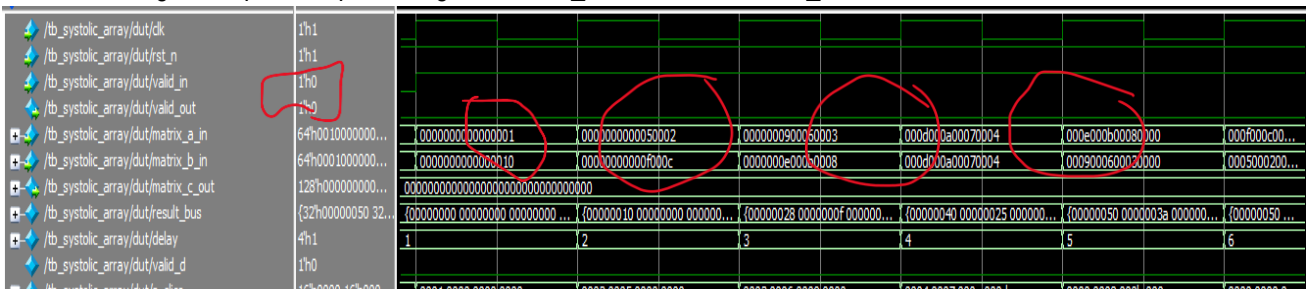


Figure 16: 4x4 Test case indicating data entry flow

As shown in fig , when the inputs are finished the valid_out will be enabled so that the design will output matrix c row by row at each posedge then when the output finished its valid output multiplied then the valid_out will dis enabled again.

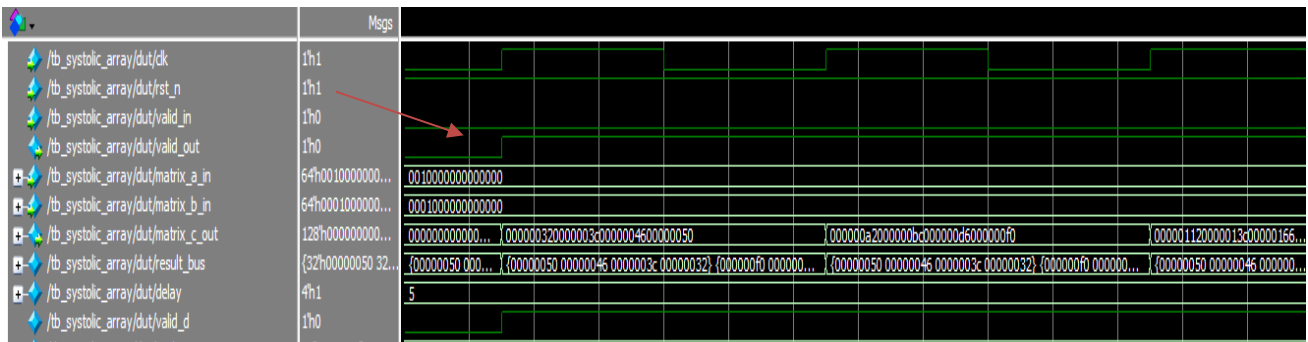


Figure 17: 4x4 test case indicating the output transition

The rows are got in hex in the fig:

- 000000320000003c0000004600000050 → 80 70 60 50
- 000000a2000000bc000000d6000000f0 → 240 214 188 162
- 000001120000013c0000016600000190 → 400 358 316 274
- 00000182000001bc000001f600000230 → 560 502 444 386

Which are the expected results. The Output Results as shown in the log file indicating the inputs matrixes and the expected and actual results so correct output results.

```

# --- Test Case: 4x4 Matrix Multiplication ---
# Matrix A:
#  1  2  3  4
#  5  6  7  8
#  9 10 11 12
# 13 14 15 16
# Matrix B:
# 16 15 14 13
# 12 11 10  9
#  8  7  6  5
#  4  3  2  1
# Expected Result (A * B):
#   80   70   60   50
#  240  214  188  162
#  400  358  316  274
#  560  502  444  386
# Collecting matrix outputs...
# Row 0 collected: 000000320000003c0000004600000050
# Row 1 collected: 000000a2000000bc000000d6000000f0
# Row 2 collected: 000001120000013c0000016600000190
# Row 3 collected: 00000182000001bc000001f600000230
# All 4 rows collected successfully!
# === Output Results ===
# Actual Result Matrix:
#   80   70   60   50
#  240  214  188  162
#  400  358  316  274
#  560  502  444  386
# --- Verification ---
# SUCCESS: All results match expected values!

```

Snippet 15: 4x4 Log file

4. 5x5 Matrices

As shown in fig , when the user has to apply the inputs matrixes then the valid_in will be enabled so at each posedge of cycles the inputs will entering.

When the inputs are finished so the valid_in will dis enabled

 


Figure 18: 5x5 Test case indicating the enable of valid_in and data entry flow

As shown in fig , when the inputs are finished the valid_out will be enabled so that the design will output matrix c row by row at each posedge then when the output finished its valid output multiplied then the valid_out will dis enabled again.

 


Figure 19: 5x5 test case indicating the output transition

The Output Results as shown in the log file indicating the inputs matrixes and the expected and actual results so correct output results.

```
# Matrix A:
#   1  2  3  4  5
#   6  7  8  9 10
#  11 12 13 14 15
#  16 17 18 19 20
#  21 22 23 24 25
# Matrix B:
#   25 24 23 22 21
#   20 19 18 17 16
#   15 14 13 12 11
#   10  9  8  7  6
#    5  4  3  2  1
# Expected Result (A * B):
#   175  160  145  130  115
#   550  510  470  430  390
#   925  860  795  730  665
#  1300 1210 1120 1030  940
#  1675 1560 1445 1330 1215
# Row 0 collected: 000000730000008200000091000000a0000000af
# Row 1 collected: 00000186000001ae000001d6000001fe00000226
# Row 2 collected: 00000299000002da0000031b0000035c0000039d
# Row 3 collected: 000003ac0000040600000460000004ba00000514
# Row 4 collected: 000004bf00000532000005a5000006180000068b
# === Output Results ===
# Actual Result Matrix:
#   175  160  145  130  115
#   550  510  470  430  390
#   925  860  795  730  665
#  1300 1210 1120 1030  940
#  1675 1560 1445 1330 1215
# SUCCESS: All results match expected values!
```

Snippet 16: 5x5 Log file

And so on for any $N_SIZE * N_SIZE$ matrixes thus it is generic parametrized with any dimension you need.

Conclusion

The systolic array architecture presented here offers an efficient and scalable solution for hardware-accelerated matrix multiplication. By leveraging a network of simple, interconnected processing elements and a carefully data flow, it achieves high parallelism and throughput, making it ideal for applications requiring intensive linear algebra computations. The modular design, with parameterized DATAWIDTH and N_SIZE , allows for flexibility in adapting the array to various matrix dimensions and data precision requirements.
